

AGING AND IN-CIRCUIT CHARACTERIZATION OF ALUMINUM ELECTROLYTIC CAPACITORS

Marcus Sonst
Application Engineer Power Management

ROHDE & SCHWARZ

Make ideas real





CONTENT

- ▶ Aluminum Electrolytic Capacitors In AC-DC Power Converter
- ▶ Common Circuits For Offline AC-DC Power Supplies
- ▶ Capacitance Calculation And Equivalent Series Resistance Fundamentals
- ▶ Basic and Extended Circuit Simulation

- ▶ Measurement Hardware
- ▶ In-Circuit Measurement And Results – Capacitance, ESR and Current Ripple
- ▶ Lifetime Prediction
- ▶ Conclusion

AL-ELECTROLYTIC CAPACITORS IN AC-DC POWER SUPPLIES

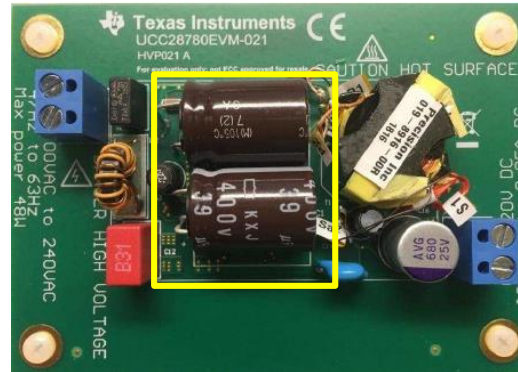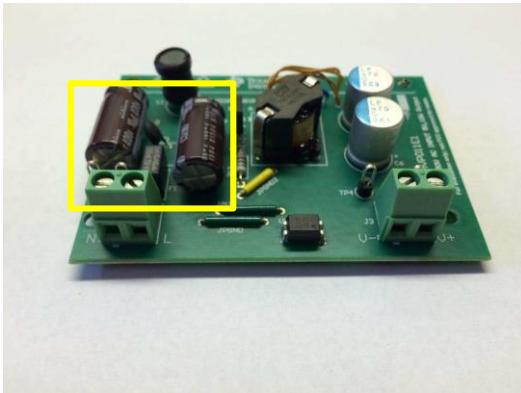- ▶ It Is Still The Key Component In Power Supplies For Several Reasons
 - Provide Large Capacitance At Higher Voltage
 - Very Price Attractive
 - Volume Per μF Is Very Good



- ▶ Aluminum Electrolytic Capacitor Is The Relevant Component Of The Overall PSU Life Time!!!!

AGING EFFECTS OF AL-ELECTROLYTIC CAPACITOR

► Impacts On Aging Of Aluminum Electrolytic Capacitors Are:

- **Temperature**

- Loss Of Electrolytic
- Leakage Current >> Oxide Degradation

- **Ripple Current**

- Local Heating >> Loss Of Electrolytic



- **Voltage**

- Leakage Current

Loss Of Capacitance And An Increasing Equivalent Series Resistors (ESR)


LINEAR POWER SUPPLY CIRCUIT

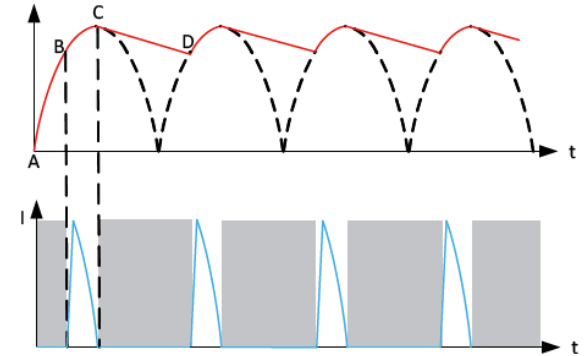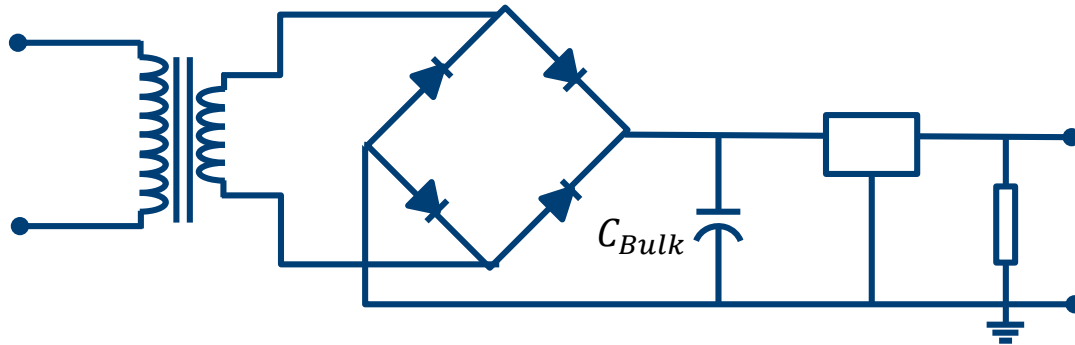- ▶ They Still Need A Storage Element To Smooth The Rectified Pulsating Voltage (Low frequency) After The Bridge Rectifier
- ▶ Use Of The Large Bulk Capacitor Based On Aluminum Electrolytic Technology Is The Preferred Choice



SWITCHING-MODE POWER SUPPLY CIRCUIT

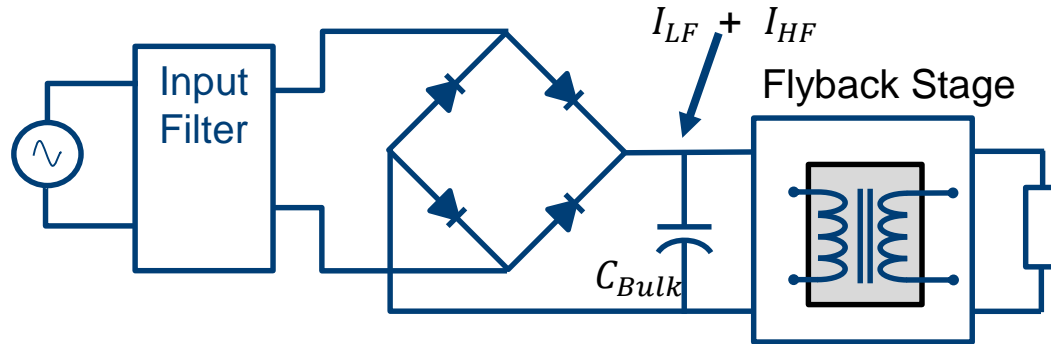- ▶ In Many Applications, Overall Efficiency Requires The Use Of Power Supplies Based on SMPS principle
 - The Bulk Capacitor Is Still Required For Smoothing The Pulsating DC Voltage
 - An Additional HF Current Component Has To Be Considered




$$I_{eff} = \sqrt{\frac{I_{LF}^2}{K_{LF}^2} + \frac{I_{HF}^2}{K_{HF}^2}}$$

The Maximum Current Ripple Is Typically Defined At Line Frequency (100Hz)

EMI OPTIMIZED POWER SUPPLY CIRCUIT

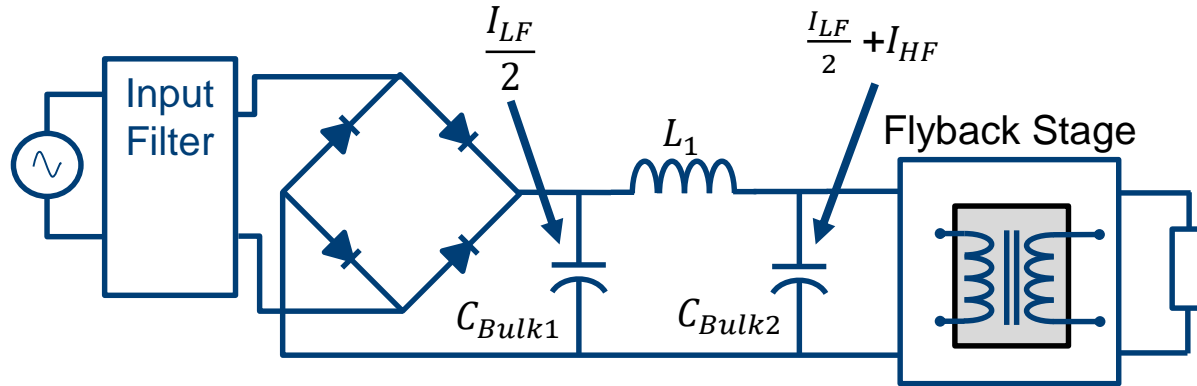- ▶ A Small Change In The Previous Setup May Solve EMI Challenges
 - An Additional Bulk Capacitor And Filter Inductor Is Used To Create A PI Filter
 - Low Frequency Content Will Flow In Both Capacitors
 - Low And High Frequency Content Will Flow Only In C_{bulk2}



Lifetime Of Bulk Capacitors Are Different!!

HOW TO CALCULATE CAPACITANCE FROM MEASURED CURRENT AND VOLTAGE

► Basic Math Fundamentals

The Integral Of The Current Over Time Can Be Expressed As The Charge


$$Q = \int_{t_1}^{t_2} i(t) dt \text{ [As]}$$

The Voltage Across The Capacitor Is Expressed By The Integral And The Scale Factor C (Capacitance)

$$u(t) = \frac{1}{C} * \int_{t_1}^{t_2} i(t) dt$$

The Capacitance Can Be Expressed Using The Formulas Above


$$C = \frac{\Delta Q}{\Delta U}$$

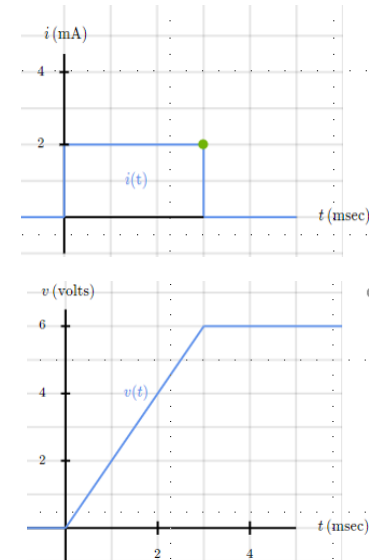

ESR CALCULATION AT SWITCHING FREQUENCY

- ▶ Impedance Of Electrolytic Capacitor


$$Z = \sqrt{ESR^2 + X_C^2}$$

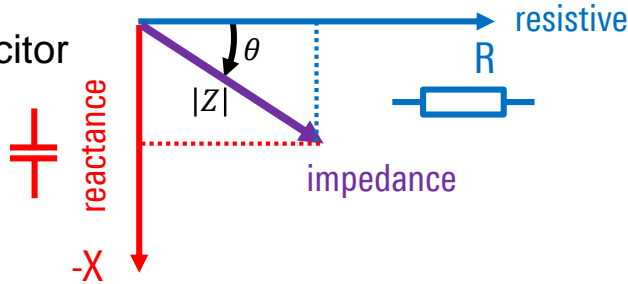

- ▶ Capacitive Reactive Can Be Neglected At Switching Frequency

$$Z = \sqrt{ESR_{fsw}^2 + X_{C_{fsw}}^2} \cong ESR_{fsw}$$
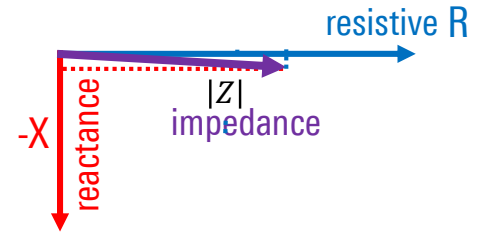
$$X_{C_{fsw}} = \frac{1}{2 * \pi * f_{sw} * C}$$




- ▶ ESR Can Be Calculated From Voltage And Current Switching Peak To Peak


$$Z = \frac{U_{C_{fsw}}}{I_{C_{fsw}}}$$

$$ESR_{fsw} = \frac{U_{C_{fsw}}}{I_{C_{fsw}}} = \frac{U_{C_{fsw_peak}}}{I_{C_{fsw_peak}}}$$

BASIC CIRCUIT SIMULATION – LF RIPPLE

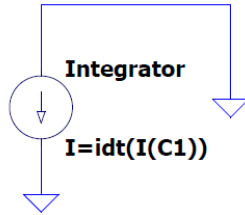

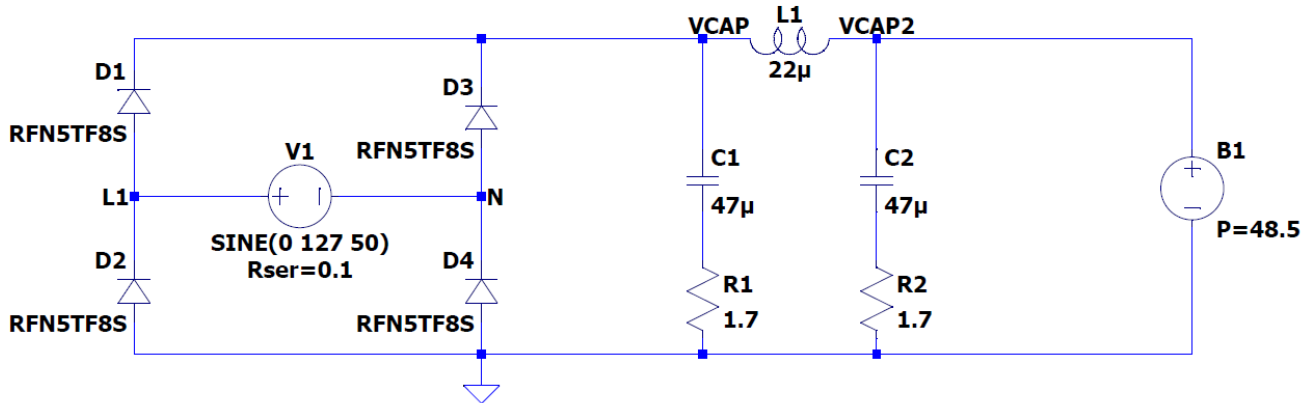
```
.options numdgt = 7
.options plotwinsize = 0
.four 100 10 10 V(VCAP)
.four 100 10 10 I(C1)
.param dt=20ms
.meas TRAN I_INTEGRAL INTEG I(C1)/dt FROM 160ms TO 180ms
.tran 0 200m 180m 100n startup
```



SIMULATION RESULTS

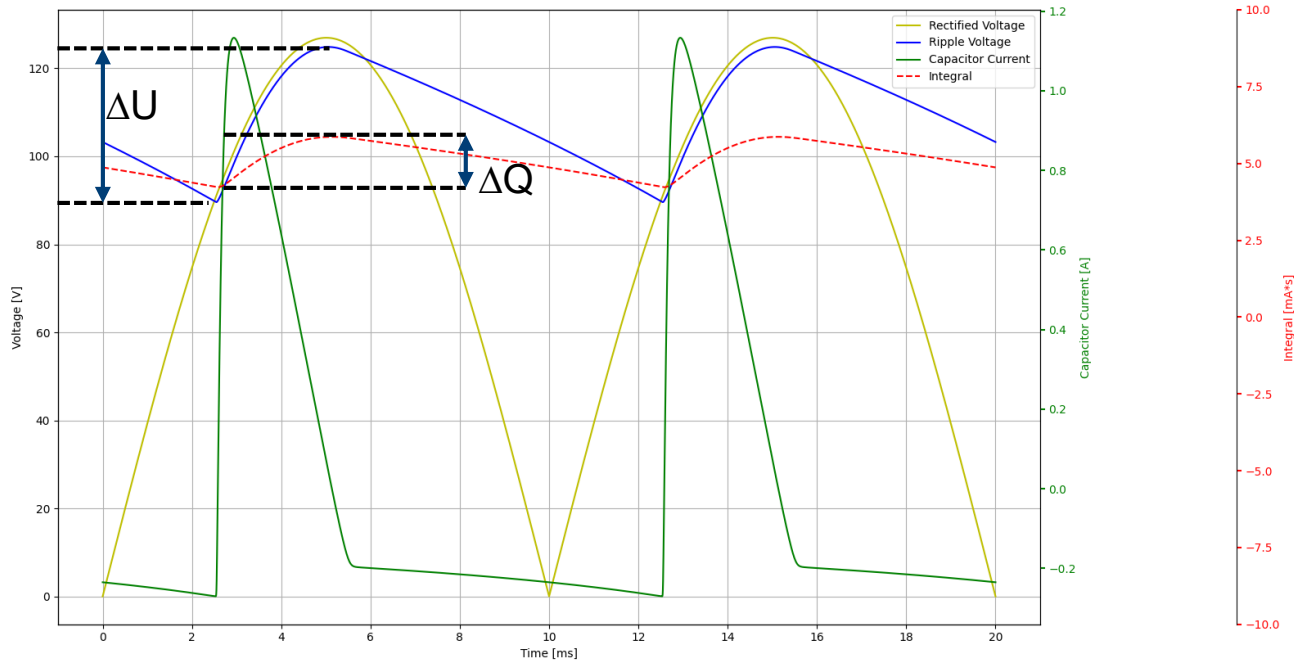► LF Ripple Simulation is used to derive RMS current and Capacitance




$$C = \frac{\Delta Q}{\Delta U} = 46,5\mu\text{F}$$

$$I_{C_RMS} = 411\text{mA}$$

EXTENDED SIMULATION CIRCUIT

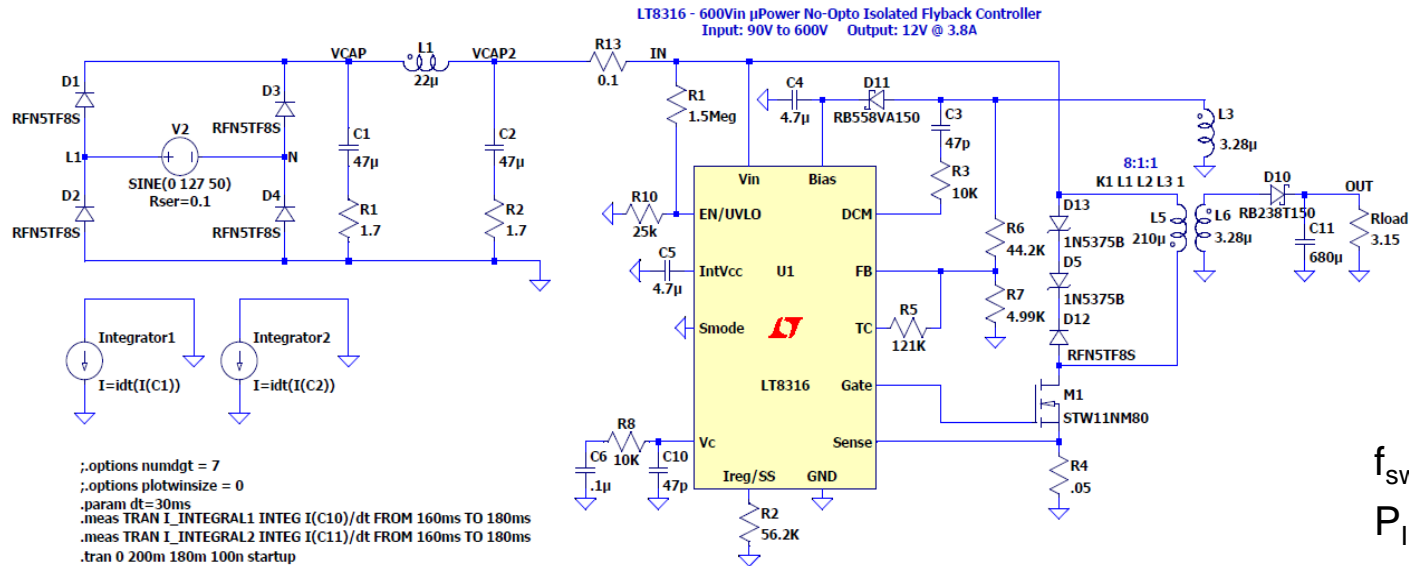- Contribution Of The Flyback Converter Has To Be Taken Into Account For Lifetime Calculation




$$f_{sw} = 100\text{kHz} \dots 110\text{kHz}$$

$$P_{IN} = 47,6\text{W}$$

SIMULATION RESULTS @ LF CAPACITOR

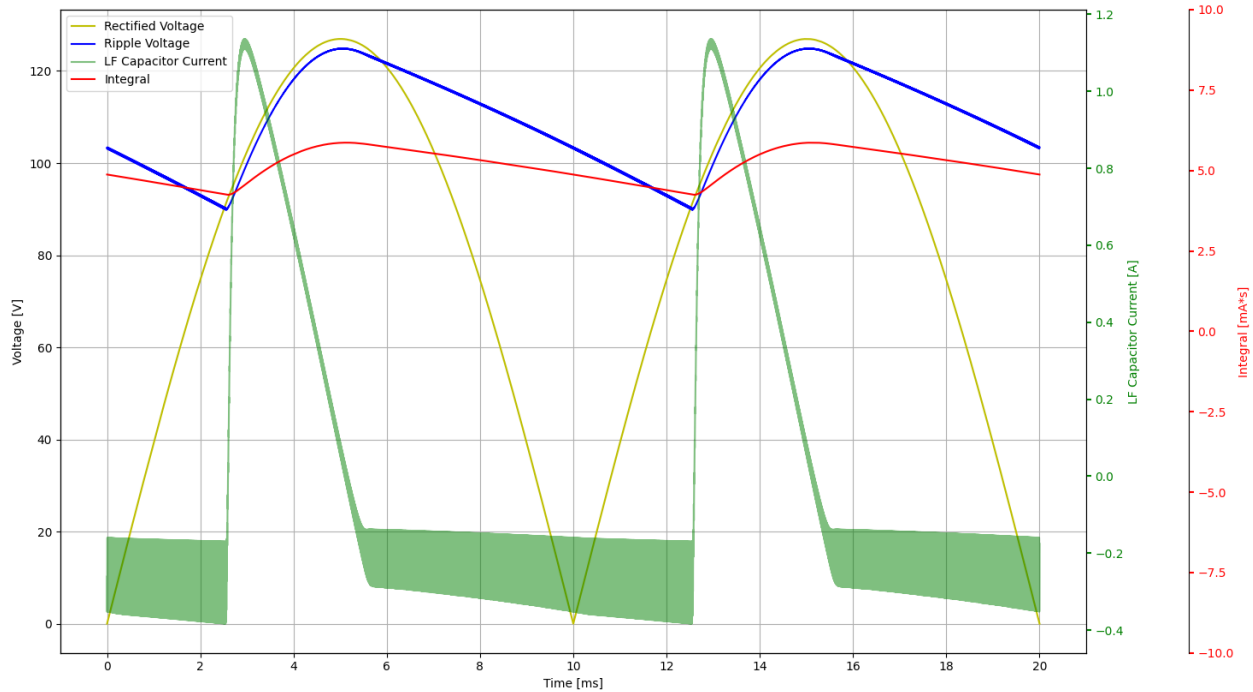
► LF Ripple Simulation To Derive RMS Current And Capacitance



$$C_{LF} = 46,3\mu\text{F}$$

$$I_{C_RMS} = 415\text{mA}$$

SIMULATION RESULTS @ HF CAPACITOR

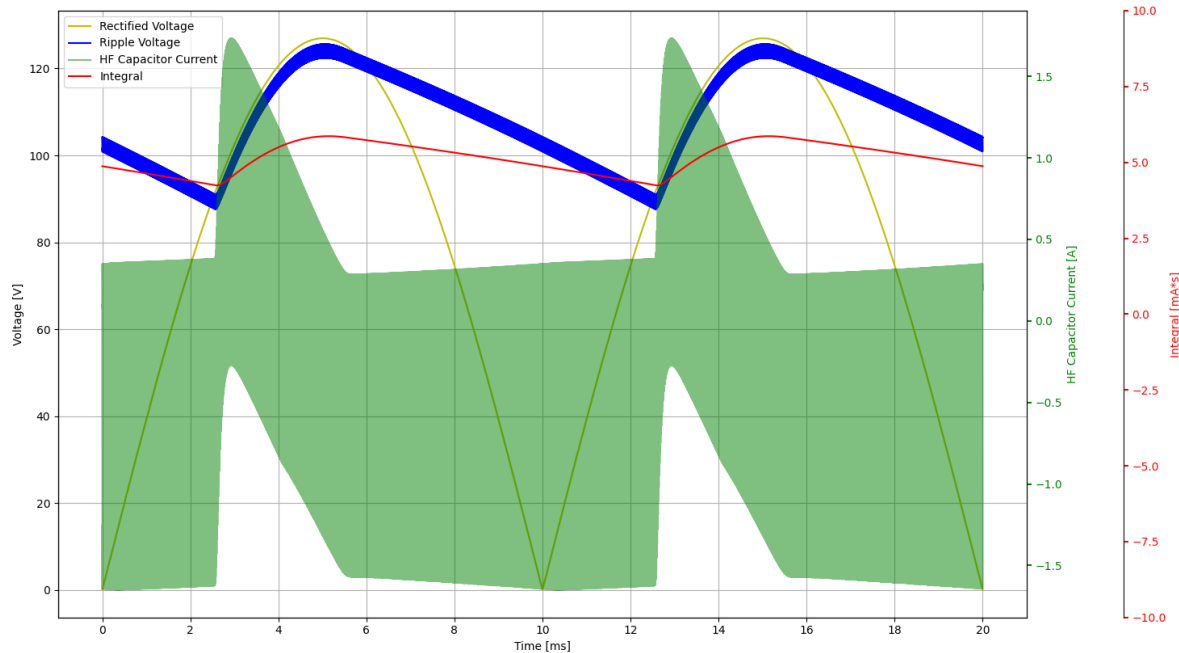



$$C_{HF} = 46,4\mu\text{F}$$

$$I_{RMS_Effective} = 741\text{mA}$$

$$I_{RMS_HF} = 688\text{ mA}$$

ESR ESTIMATION BASED ON SIMULATION DATA

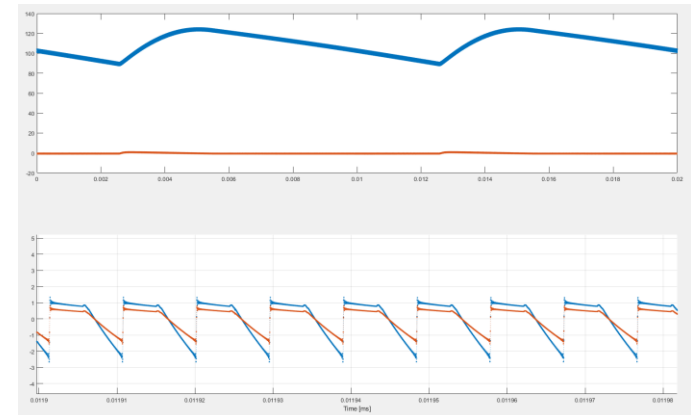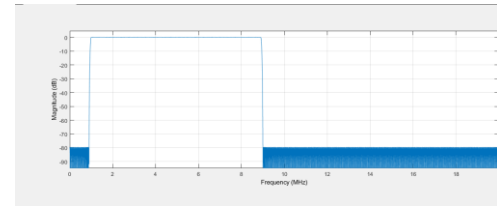- ▶ Digital FIR Filter (Band Pass Filter) Can Be Used To Measure Peak To Peak At Switching Frequency
- ▶ Filter Design Is Based On Matlab Filter Designer
- ▶ ESR Calculation Within Matlab



$$ESR_{f_{sw}} = \frac{U_{C_{fsw_peak}}}{I_{C_{fsw_peak}}} = \frac{4.133 V}{2.435 A} = 1.697 \Omega$$



Very Close To The Simulation Model!!

PROBING

- ▶ What Kind Of Hardware Is Required To Derive The Capacitance, Ripple Current And ESR Value Within The Circuit Operation.
 - *High Voltage Differential Probe*
 - R&S ZHD07 - Offset Capability And Sufficient Bandwidth
 - *Current Probe*
 - Current Clamp Probe or Rogowski Probe
 - R&S RT-ZC20B Offers Very Good Bandwidth
 - Rogowski Probe Is easy To Attach To The Circuit (AC Current Only)



OSCILLOSCOPE

- ▶ An Device With The Following Characteristic Is Essential:
 - Bandwidth Of At Least 1GHz Is Required
 - Use Of Customized Digital Filter
 - Integral Math Function Should Be Used To Calculate Q Charge
 - Measurement Function Like RMS, Peak to Peak, etc.
 - Powerful Cursor Setting Supports The User To Extract The Capacitance





The RTO6 Is The Perfect Choice To Perform The Challenging Task

LCR-METER

► It Was Used To Validate The In-Circuit Measurements

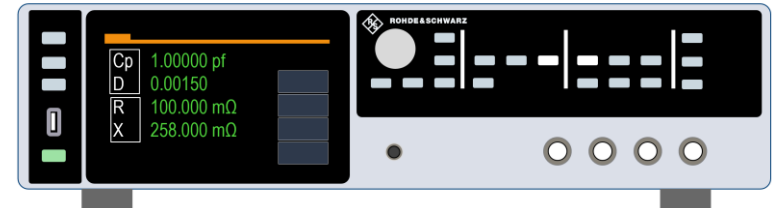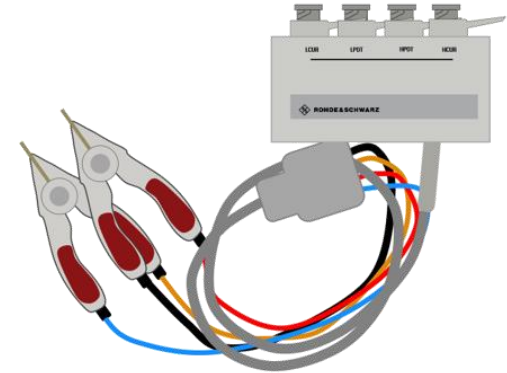- R&S LCX100/LCX200 LCR Meter Provides High Accuracy
 - Basic Accuracy Up To 0.05%
- It provides Many Different Impedance Measurement Functions
 - ESR, ESL And Capacitance Is Needed



CAPACITANCE EVALUATION PART I

► Capacitance Measurement At Line Frequency



HD Mode with BW
Limit 10kHz (16Bit)

$$C = \frac{\Delta Q}{\Delta U} = \frac{603 \mu A * s}{13.24 V} = 45,5 \mu F$$

DUT Parameter:
230VAC @ Iout = 20V/2A

CAPACITANCE EVALUATION PART II

► A Combination Of Low and High Frequency Content Is Present



HD Mode With BW
Limit 10kHz (16Bit)
(Switching Frequency
Rejection)

$$C = \frac{\Delta Q}{\Delta U} = \frac{625 \mu A * s}{13,4 V} = 46,7 \mu F$$

DUT
230VAC @ Iout = 20V/2A

RIPPLE CURRENT MEASUREMENT PART 1

► Ripple Current Measurement At Line Frequency



HD Mode with BW
Limit 50MHz (16Bit)

$$I_{RMS_LF} = 254 \text{ mA}$$


$$I_{RMS_Total} = 255 \text{ mA}$$

DUT

230VAC @ Iout = 20V/2A

RIPPLE CURRENT MEASUREMENT PART II

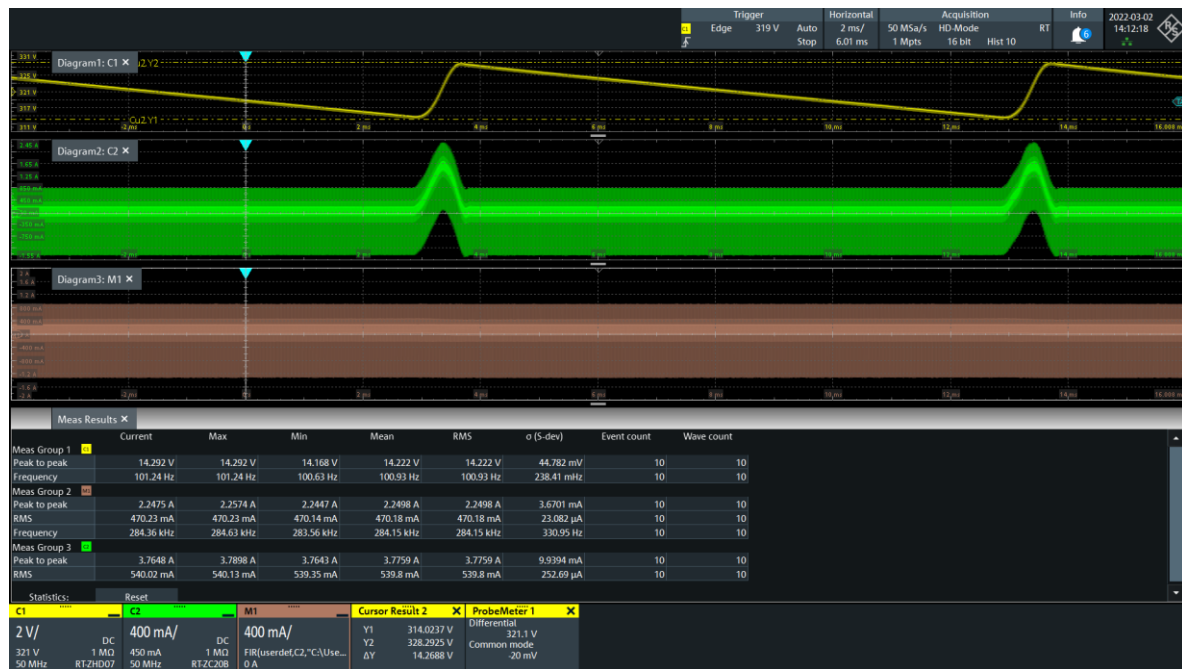- Ripple Current Measurement At Line Frequency, Switching Ripple And The Total Ripple



HD Mode with BW
Limit 50MHz (16Bit)

$$I_{\text{RMS_LF}} = 265 \text{ mA}$$

$$I_{\text{RMS_Total}} = 540 \text{ mA}$$

$$I_{\text{RMS_HF}} = 470 \text{ mA}$$

DUT

230VAC @ $I_{\text{out}} = 20\text{V}/2\text{A}$

ESR IN-CIRCUIT MEASUREMENT @ SWITCHING FREQUENCY

► Ripple Voltage And Current Measurement At Switching Frequency



Results (@25°)

$$U_{PP} = 1,02 \text{ V}$$

$$I_{PP} = 1,85 \text{ A}$$

$$\text{ESR} = 551 \text{ m}\Omega$$

$$F_{sw} = 285 \text{ kHz}$$

Bandpassfilter (FIR)

$$F_{stop1} = 13 \text{ kHz}$$

$$F_{pass1} = 125 \text{ kHz}$$

$$F_{pass2} = 11 \text{ MHz}$$

$$F_{stop2} = 11,25 \text{ MHz}$$

CAPACITANCE AND ESR COMPARISON

	In-Circuit Measurement		LCR-Bridge Measurement		Failure [%]	
	LF-Cap @ 100Hz	HF-Cap @ 100Hz	LF-Cap @ 1kHz	HF-Cap @ 1kHz	LF-Cap	HF-Cap
Capacitance [μ F]	45,5	46,7	43,4	43,8	4,6	6,2
Capacitance [μ F] (2000 h)	44,0	43,1	41,3	41,5	6,1	3,7
ESR [Ω] @ 285 kHz	X	0,55	0,710	0,628	X	-13
ESR _{2000h} [Ω] @ 285 kHz	X	2,91	4,049	3,619	X	-24

RIPPLE CURRENT AND TEMPERATURE RESULTS

Position	Current Type [mA]	In-circuit Measurement		T _{core} [°C]		T _a [°C]
		LF-Cap	HF-Cap	LF- Cap	HF-Cap	
New Capacitor	I _{RMS_Total}	255	540	39,9	42,2	25,6
	I _{RMS_HF}	X	470			
	I _{RMS_LF}	254	265			

LIFETIME CALCULATION

► Based On Core Temperature Measurement

Lifetime Calculation (Law of Arrhenius)

$$L_x = L_0 * 2^{\left[\frac{T_0 - T_a}{10}\right]}$$

$$L_0 = 10000h$$

$$T_0 = 105^\circ\text{C}$$



Lifetime Calculation With New Device

$$L_{x_LF} = 911\,392\,h$$

$$L_{x_HF} = 777\,084\,h$$

Lifetime Calculation With Accelerated Aging

$$L_{x_LF} = 530\,764\,h$$

$$L_{x_HF} = 458\,865\,h$$

Most Accurate Calculation But It Requires A Built-In Thermocouple Element

LIFETIME ESTIMATION

► Based On Ripple Current Measurement

Current Ripple Including Frequency Multiplier

$$I_{eff} = \sqrt{\frac{I_{LF}^2}{K_{LF}^2} + \frac{I_{HF}^2}{K_{HF}^2}}$$

$$K_{LF} = 0,5$$

$$K_{HF} = 1$$

$$I_{eff_LF_cap} = 510mA$$

$$I_{eff_HF_cap} = 756 mA$$

Temperature Rise And Lifetime Estimation

$$\Delta T = \Delta T_{max} * \left(\frac{I_{eff}^2}{I_{Rated}^2} \right)$$

$$I_{Rated} = 1050 mA$$

$$\Delta T_{LF} = 1,2 K$$

$$\Delta T_{HF} = 2,6 K$$

$$K_{Ripple} = 2^{\left[\frac{\Delta T_{max} - \Delta T}{5} \right]}$$

$$K_{Ripple_LF} = 1,693$$

$$K_{Ripple_HF} = 1,454$$

$$\Delta T_{Max} = 5K$$

$$L_x = L_0 * 2^{\left[\frac{T_0 - T_a}{10} \right]} * K_{Ripple}$$

$$L_{x_LF} = 1\,532\,328 h$$

$$L_{x_HF} = 1\,316\,010 h$$

$$T_0 = 105^\circ C$$

Frequency [Hz]	120	1000	10000	≥ 100000
Multiplier	0.50	0.80	0.85	1.0

40°C Should Be Considered For Ta, If The Ambient Temperature Is Below 40°C

CONCLUSION

- ▶ Smart Circuit Simulation Will Provide The First Insight Of Key Values But Cannot Avoid Real Measurements
- ▶ In-Circuit Measurement Supports The Designer With RMS Ripple Current Measurement To Estimate Lifetime Of An Capacitor In An Easy Way But Is Limited In Accuracy
- ▶ A Core Temperature Measurement Of The Capacitors Operating In The Application Provides Best Accuracy But Requires More Effort
- ▶ In addition, In-Circuit Measurement Provide Capacitance and ESR Values Within the Application.
- ▶ LCR-Bridge Measurement Provides Highest Accuracy For Capacitance And ESR Measurements
- ▶ Lifetime Calculation Of Aluminum Electrolytic Capacitor Is Essential To Estimate The Overall Power Converter Lifetime

THANK YOU

The background of the slide is a dark navy blue. On the right side, there are several parallel diagonal stripes in a slightly lighter shade of blue, creating a sense of movement and depth. The stripes run from the top right towards the bottom left.

RIPPLE CURRENT AND TEMPERATURE RESULTS

Position	Current Type [mA]	In-circuit Measurement		T _{core} [°C]		T _a [°C]
		LF-Cap	HF-Cap	LF- Cap	HF-Cap	
New Capacitor	I _{RMS_Total}	255	540	39,9	42,2	25,6
	I _{RMS_HF}	X	470			
	I _{RMS_LF}	254	265			
<i>Used Capacitor (2000h)</i>	<i>I_{RMS_Total}</i>	<i>232</i>	<i>299</i>	<i>47,4</i>	<i>49,8</i>	<i>25,6</i>
	<i>I_{RMS_HF}</i>	<i>X</i>	<i>217</i>			
	<i>I_{RMS_LF}</i>	<i>232</i>	<i>207</i>			

ESR IN-CIRCUIT MEASUREMENT ACCURACY

► < 5% failure must be accepted

$$ESR * 1.05 > \sqrt{ESR^2 + X_C^2}$$

$$ESR^2 + \left(\frac{1}{2\pi fC}\right)^2 < 1.1025 * ESR^2$$

$$\frac{1}{f * C} < 2.0116 * ESR$$

$$f > \frac{1}{2.0116 * ESR * C}$$

$$f > \frac{1}{2.0116 * 1.7 * 47 \mu F} = 6.22 kHz$$