
Benefits of Million Times Larger Capacitance in EDLCs: Supercapacitor Assisted Novel Circuit Topologies

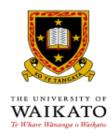Nihal Kularatna
School of Engineering
The University of Waikato
Hamilton
New Zealand







Presentation outline

- Designer's view point on supercapacitors with a summary on traditional applications
- Non traditional supercapacitor applications Supercapacitor Assisted (SCA) techniques
- High efficiency linear DC-DC converters at extra low frequencies -[SCALDO technique]
- Supercapacitor based high performance surge absorbers- [SCASA technique]
- Supercapacitor based rapid water heaters [SCATMA technique]
- SC energy storage for DC microgrid applications [SCALED technique]
- SC assisted high density inverters [SCAHDI technique]
- How simple resistor-capacitor charging loop theory is extended in SCA techniques –
 [SCALoM theory]
- Conclusion



Normal capacitors and their limits

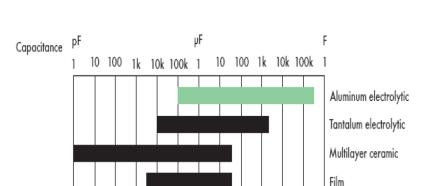


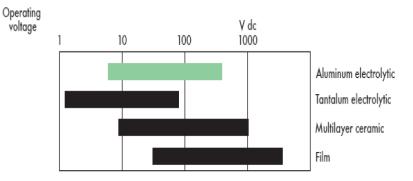

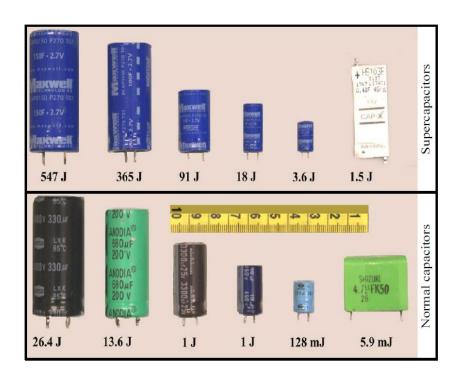2. Common dielectric materials, i.e., aluminum oxide, tantalum tetroxide, titanium oxide barium, and polyester polypropylene, also pose limits on capacitance level and operating-voltage capabilities.

Source: Dirjish, M., Ultracapacitors branch out to wider markets, Electronic Design, On line ed. Nov 17, 2008


Physical Comparison of Supercapacitors (SC) and Electrolytic Capacitors




Typically, in SCs we get approximately one million times bigger capacitance, but at the penalty of very low DC voltage rating

SC is an electric double layer device

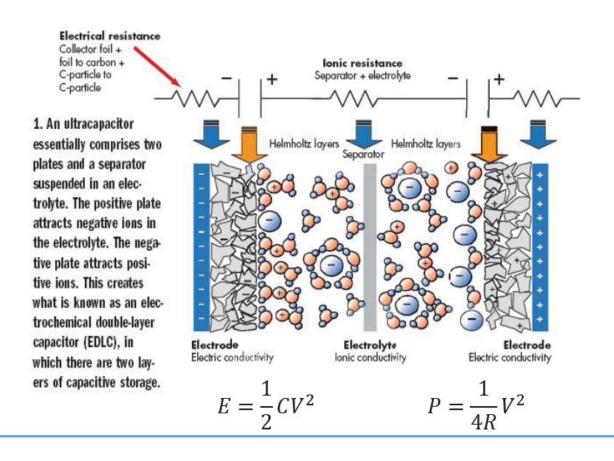• Inside a SC two capacitors are formed in series



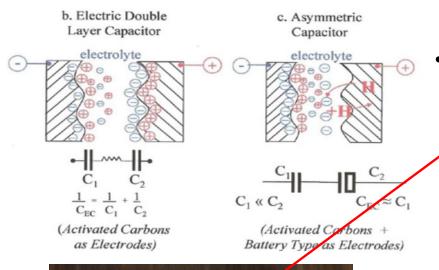Supercapacitors versus Hybrid Supercapacitors



Early versions were symmetrical double layer capacitors [3.7Wh epergy capability example]


Then hybrid devices with one electrode similar to Li-ion batteries were commercialized [8.2Wh energy capability example]

Green-Cap
EDLC (DV)
3.0V 3000F

Source: Samwha Electric

More recently capacitor-batteries were introduced [40 Wh energy capability example]

Ragone plot

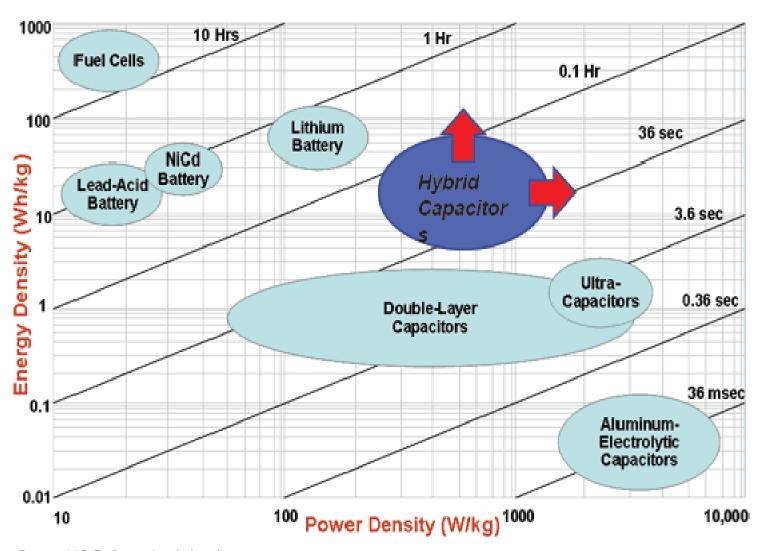

Source US Defence Logistics Agency

Comparison of practical devices


Image	Device Type	Manufacturer	Capacitance	Voltage Rating	ESR (mΩ)	Total Energy Storage Capability	Maximum possible output power (load resistance=ESR)
O MARIANAM O	Supercapacitor	LS Mtron	3000 F	2.7 V	0.36	10.9 kJ	6.07 kW
	Electrolytic capacitor	Cornell-Dubilier	2200 μF	50 V	71	2.75 J	8.8 kW
	Hybrid supercapacitor	Samwha Electric	7500 F	2.8 V	0.8	29.4 kJ	2.45 kW
Freigizer 🚊	Disposable energizer cell –C type	Energizer	8.35 Ah	1.5 V	324 mΩ	45.1 kJ	1.73 W
1603 3650043 71	Li-ion cell	Panasonic	3.4 Ah	3.6 V	50 mΩ	11.52 kJ	64.8 W

5/4/2020 7

A broad comparison – Key specifications based

	Power Density	Energy Density	Cycle life	Temperature range
Li-ion battery	3 kW/kg	200 wh/kg	500-1000	0°C- 60° C
Symmetrical SC	10 kW/kg	10 Wh/kg	500,000 to 1,000,000	- 40°C- 60° C
Hybrid SC	5kW/ kg	25 Wh/kg	10,000 - 50,000	-20°C- 60° C

Battery versus SC

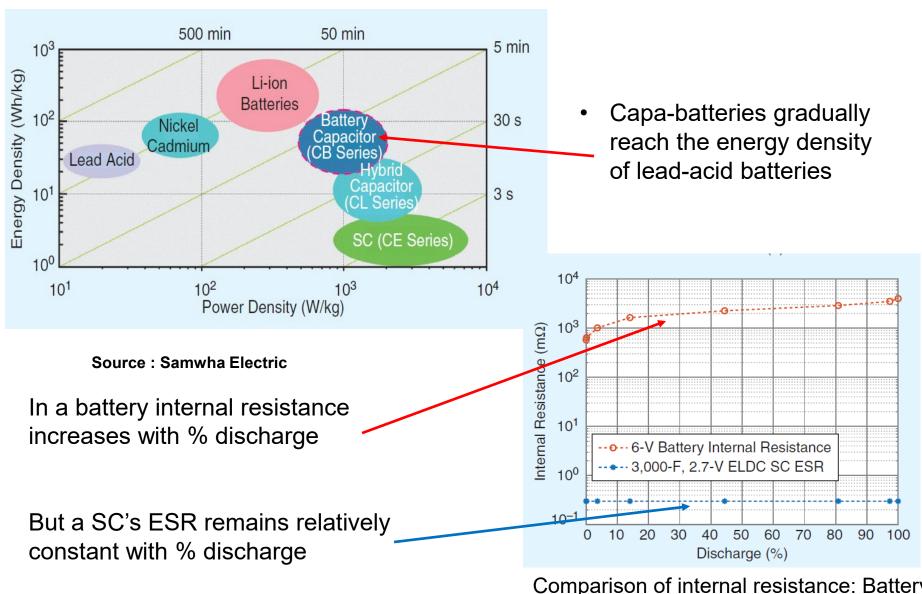

Comparison of internal resistance: Battery versus SC

Traditional Applications of Supercapacitors

- •In general supercapacitors have much less energy density than batteries
- •But their power delivery capability (Watts/kg) is quite high compared to batteries
- •Large supercapacitors have very low ESR in the range of few m Ω s to fractional m Ω s

Common supercapacitor applications are in


- UPS systems
- Wind turbine systems
- Electric vehicles/ Fork lifts/ Hybrid buses
- Utility voltage stabilizer systems
- Photo voltaic systems
- Memory back up systems
- In many of these applications battery-supercapacitor hybrid systems are used

Non traditional applications of supercapacitors

Supercapacitor Assisted (SCA) Techniques

Capacitors in simple DC blocking circuits

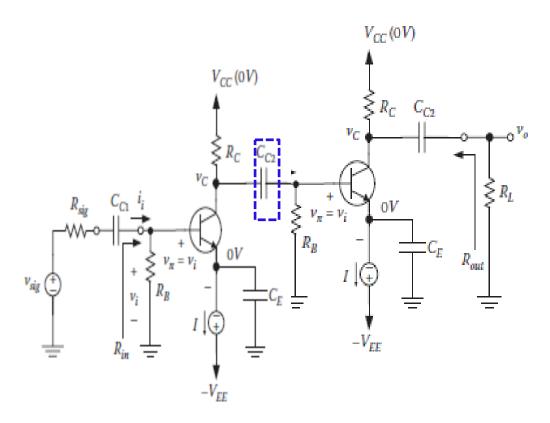- We use electrolytics and ceramics as DC blocking elements
- Typical values used are from fenano-farads to tens of microfarads
- When a circuit is powered, blocking capacitor charges to t difference in voltages within micro to millisecond time perio
- If we replace a 1 µF capacitor with a 1 F capacitor the circuit take one million times longer to reach its steady state of blocking!



This gives you a different starting point to think of using the SCs in circuits more creatively!

Supercapacitor as a lossless voltage dropper – for high efficiency linear DC-DC converters

Vout

Series-Pass

out

Device

Control

Circuit

 A linear DC-DC converter is based on an energy dissipating series transistor


However, they are very inefficient

- •12-5V converter has a theoretical maximum efficiency of 42%
- •5-3.3 V converter gives you only 66% efficiency —
- •Efficiency is given by $\frac{V_o}{V_{in}}$
- If you insert a resistor in the series path energy dissipated in transistor can be part-transferred to the resistor
- However the overall efficiency will not improve!

If a large capacitor is used instead of the resistor, it will store energy while dropping the voltage difference across transistor

Supercapacitor Assisted Low Dropout Regulator (SCALDO) technique

- A capacitor carrying a charge or discharge current of I_L for a time period of Δt changes the voltage across the capacitor by $I_L \Delta t$
- If the capacitor is very large this ∆V will be very small
- A supercapacitor (one million times larger than an electrolytic), will not be fully charged for a long time to block the circuit
- In supercaps, ESR is very small and this causes only a negligible voltage drop across ESR
- In larger SCs ESR can be significantly lower than the on resistance of commonly used MOSFETs

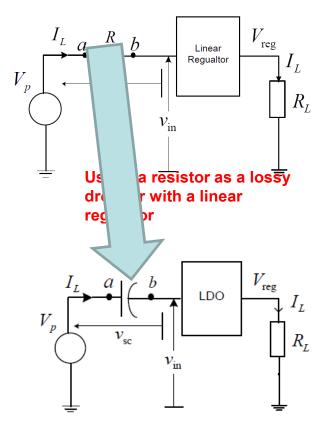

Use of a supercap as a lossless dropper with an LDO

This allows us to use SCs as lossless droppers in linear power converters

Implementation of the SCALDO technique

A low dropout regulator (LDO) is a linear regulator, where input to output voltage difference is low, to keep the efficiency high.


Now let us insert a SC pre-charged to Vc in the series path ...

LDO's efficiency will be V_{reg}/V_{in} , but input voltage now is V_{in} + V_{C}

When load current, I_L is drawn through the SC its voltage keeps increasing while V_{in} keeps dropping

Given the size of the capacitor it will be a slow process, and when V_{in} drops to minimum, we can connect the capacitor to LDO directly, and disconnect the input supply (as per lower Figure)

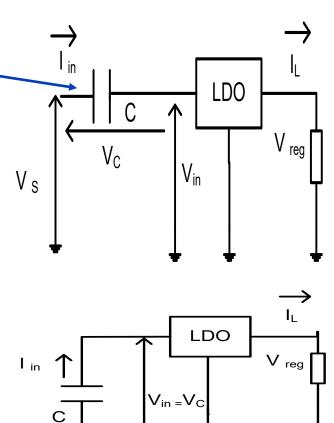
When V_c goes below V_{in} min the circuit will return to series configuration (as per upper figure)



The above approach allows us to develop a linear DC output converter with a energy recirculation frequency, typically in the range of millihertz to fractional hertz

Practical implementation of the SCALDO technique

•SCALDO technique allows you to build very high efficiency linear regulators

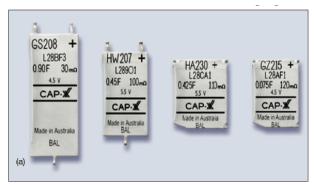


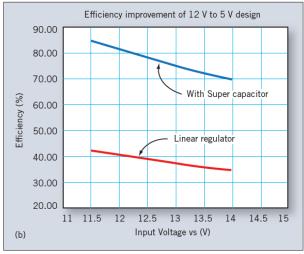


Fig. 3(a) Capacitor size reductions in an early prototype for 12-5V regulator supercaps used. (b) Shows efficiency improvements in 12-5 V regulator supercaps.

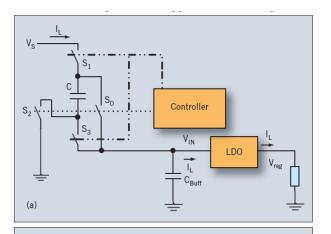


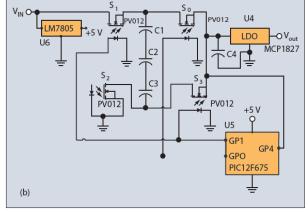


Fig. 4(a) The 12 V to 5V circuit to achieve efficiency improvements shown in Fig. 4(b). The implementation in Fig. 4(b) is shown using a PIC microcontroller.

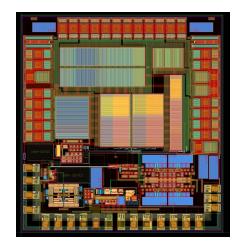

SCALDO technique in IC implementation

In a typical SCALDO circuit such as this 12-5V converter we get an efficiency improvement factor of 2

Ref: (2014) Kankanamge, K., Kularatna, N., Improving the end-to-end efficiency of DC-DC converters based on a supercapacitor assisted low dropout regulators (SCALDO) technique, IEEE Transactions on Industrial Electronics, Vol 61, Iss 1, January 2014, pp 223-230

SCALDO variations

RS-SCALDO technique for high current converters


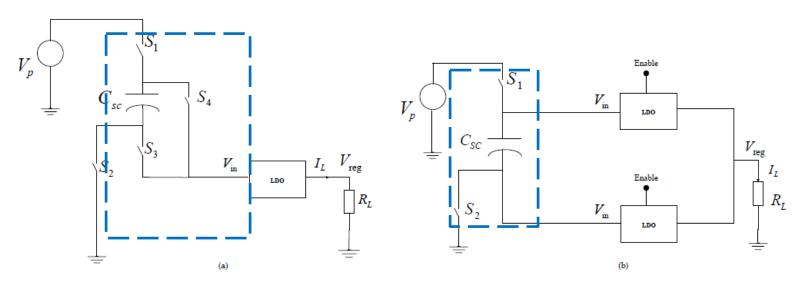


Figure 1.1: (a) Basic SCALDO configuration with single LDO and 4 switches (b) Modified RS-SCALDO (Reduced switches) configuration with two identical LDOs and two switches

By splitting the LDO into two half size LDOs we can reduce the number of powers switches

Basis for linear VRM systems!

DO SCALDO Concept for Split-Rail

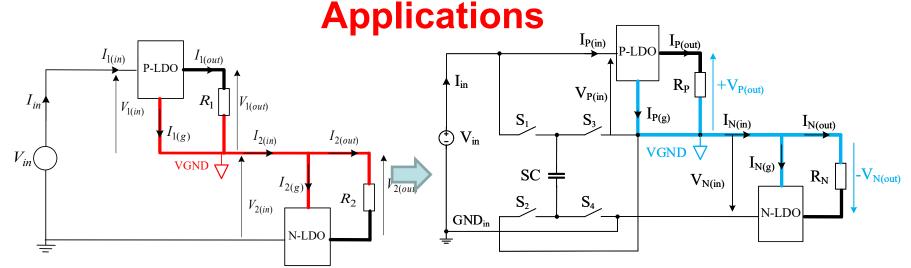

Cascaded P-LDO and N-LDO

Dual-Polarity SCALDO Technique



- ➤ End-to-end efficiency: 81 %
- > Switching frequency: 0.36 Hz
- Differential output power: 7.5 W
- ➤ Out put voltages : ± 5V
- ➤ Input voltage: 12 V DC

[•] Ref -Subasinghage, K., Gunawardane, K. & Kularatna, N. & Lie, T.K, Extending the Supercapacitor-Assisted Low-Dropout Regulator (SCALDO) Technique to a Split-Rail DC–DC Converter Application, IEEE Access, Vol 7, 2019.


A summary on SCALDO

- SCALDO is a high efficiency linear DC-DC converter
- It provides the hall marks of a linear converter, while eliminating the low efficiency of a straight linear converter
- No RFI/EMI filters needed since energy recirculation happens at fractional Hz frequency
- By over-sizing the SC DC-UPS capability can be added to the converter
- It can be extended to many applications
 - Split rail high efficiency linear converters
 - High current DC power supplies
 - 48 V Google new architecture power supplies
 - AC input based high efficiency isolated power supplies
 - Renewable energy DC-DC converters
- It is not a variation of switched capacitor converters ---[Ref -Kankanamge, K., Kularatna, N., Supercapacitor assisted LDO (SCALDO) technique-an extra low frequency design approach to high efficiency DC-DC converters & how it compares with the classical switched capacitor converters, Proc of 28th Annual IEEE-APEC-2013, pp 1979-1984.]

Surge protectors based on supercapacitors: SC Assisted Surge Absorber (SCASA) Technique

Can SCs absorb high voltage transients like lightning surges induced on power supplies?

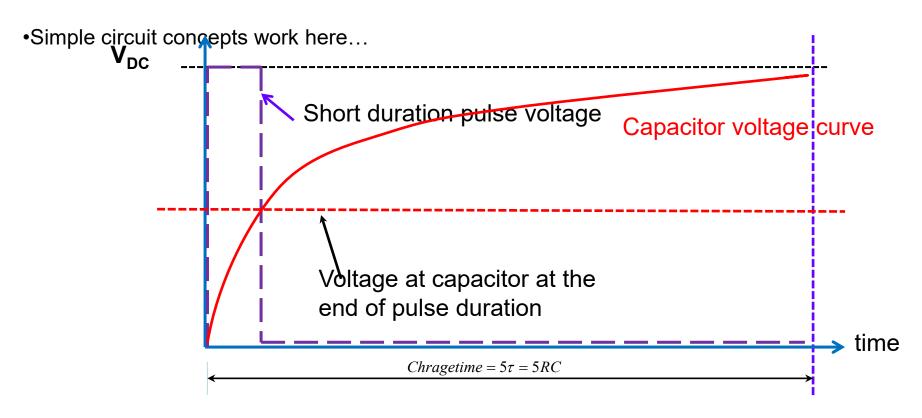- •We have tested several types of SCs for their surge absorb capability using a Lightning Surge Simulator
- Most SCs can absorb transient HV surges of several 100 micro second durations



Surge Capability Testing of Supercapacitor Families Using a Lightning Surge Simulator

Nihal Kularatna, Senior Member, IEEE, Jayathu Fernando, Amit Pandey, and Sisira James, Student Member, IEEE

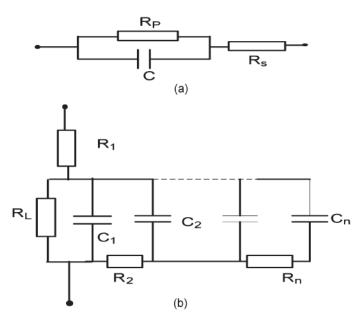


Fig. 2. SC equivalent circuits. (a) Classical equivalent circuit. (b) Ladder circuit.

Supercapacitors have very long time constants


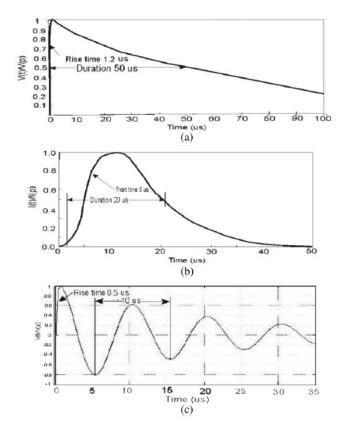


Fig. 3. Few examples of wave shapes defined in surge test standards.
(a) Open-circuit voltage waveform. (b) Short-circuit current waveform.
(c) Ring wave.

(SCASA)- concept development

- A simple low cost symmetrical SC in the range of 1 to 100 F has energy absorption capability of 3 to 400 Joules
- A typical lightning surge carries anything between few Joules to few 100 Joules.
- However, they are very low DC voltage rated devices, and can not be placed across a power line (Live to Neutral) directly like a MOV or a BBD
- Also it makes very low impedance across the terminal at 50 or 60 Hz, determined by 1/ ωC
- Given the above, a special configuration of a surge protection circuit was developed [us patent 9,466,977 B2, Power and telecommunications surge protection apparatus, Oct 2016]

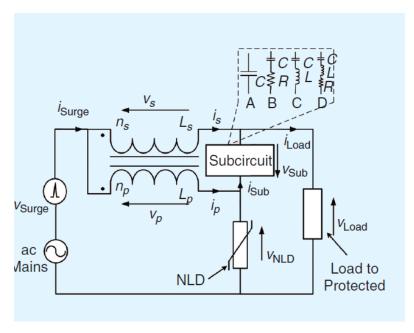


The SCASA circuit topology is based on a SC sub-circuit, combined with a coupled inductor and a typical MOV

A commercial product based on SCASA

[Courtesy of Thor Technologies, Australia]

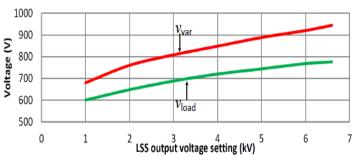- A commercial product was developed in collaboration with Thor Technologies, Australia
- This has lesser components compared to a traditional surge protector
- It satisfies UL 1449 3rd Ed test specification without component deterioration, when repeated



In SCASA, number of components are less and the transient related voltage at the protected load is less than the clamping voltage at the MOV



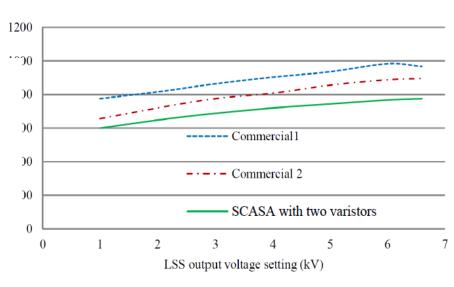


Figure 5.19: Performance comparison of SCASA with two commercial surge protectors

Supercapacitor Assisted Temperature Modification Apparatus (SCATMA): A SC based solution to hot water delay issue

Instant water heating: SCATMA

Well-known problem at water faucets

- In our home environments central water heater is at a distant location from individual faucets
- This makes cold water storage between the central heater and the faucet
- Result is delayed hot water at the faucet
- Delay can be anything from about 10 seconds to a minute depending on the length of the buried pipes
- This creates a huge waste of water, every day


Why it is not easy to solve the problem

- Maximum power we can draw from a wall socket is less than 2.5 kW
- If flowing water is to be heated fast, a 10 to 20 kW heater element is required just before the faucet
- Building heaters and tanks to do this is complex and costly
- Safety/ regulatory issues if 230, 50 Hz mains is to be wired closed to faucet [You need a voltage source lower than 70 V AC/ DC to be safe]

Energy and power requirements for rapid water heating


Flow Rate (L min ⁻¹)	4			6		
Temperature Rise (°C)	20	30	50	20	30	50
Total Energy (W h)	46	70	116	70	105	175
Average Power (kW)	5.6	8.4	14	8.4	12.6	21
Average Current at 50 V (A)	112	168	280	168	252	420


SCATMA

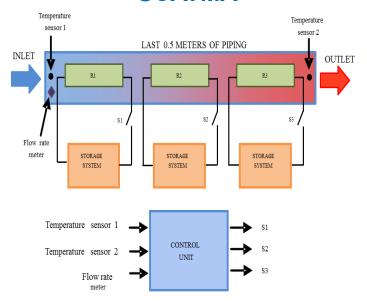


Implementation

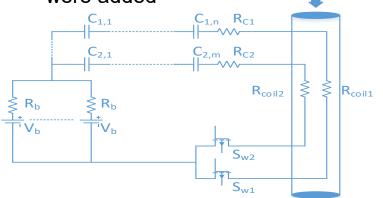- A SC bank of 50 to 150 Wh with very low ESR was developed
- It operates from a DC source less than 50 V to be safe next to a water faucet
- 10 -20 kW capable heater coil was built and placed inside the last section of plumbing before faucet
- A water fallow rate sensor and a microprocessor based control units with high current MOSFET switches were added



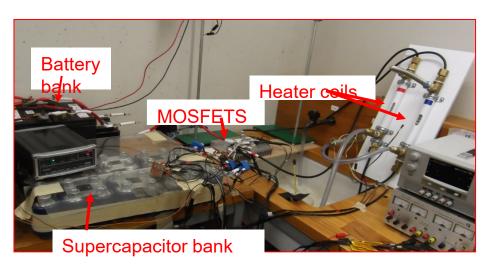

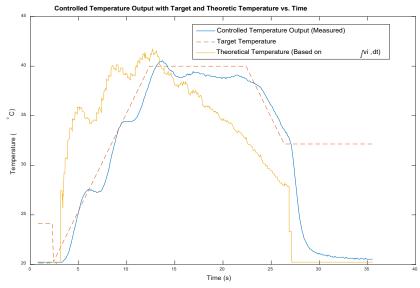

In first prototypes, to lower the cost, a battery-SC hybrid solution had to be used.

However with new hybrid SCs, SC only solution is feasible.

Is there a common theoretical concepts behind all these SCA techniques?

Answer is a BIG YES... a unique extension to our text book R-C circuit theory

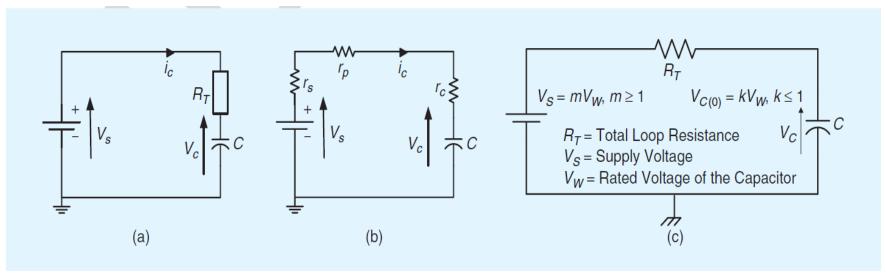


Figure 3 – The generalized case of the R–C circuit. The (a) simple textbook case with a capacitor starting from zero voltage, (b) resistive components contributing to loop resistance (R_r), and (c) the SC in a precharged condition.

- It is based on two simple concepts
 - In the simple RC circuit replace the capacitor with a supercapacitor..[Extend time constant]
 - Add a useful resistive load, a heater, DC-DC converter, inverter or any power electronic building block (PEBB) [To consume losses in resistor of RC circuit]

Then by modifying the power source by a *factor m* and keeping the capacitor precharged with *factor k* (as in Figure 3(c)), you achieve SCA- Loss management theory

SCALoM Theory

- All what we achieve is the reduction of losses in parasitic components of the RC circuit
- And, extending the circuit time constant by several orders due to supercapacitor for low speed operation for less dynamic losses

Ref: Kularatna, N. & Jayananda, D., Supercapacitor Based Long Time Constant Circuits: A Unique Design Opportunity for New Power Electronic Circuit Topologies, IEEE Industrial Electronics Magazine, June 2020 issue (In print process).


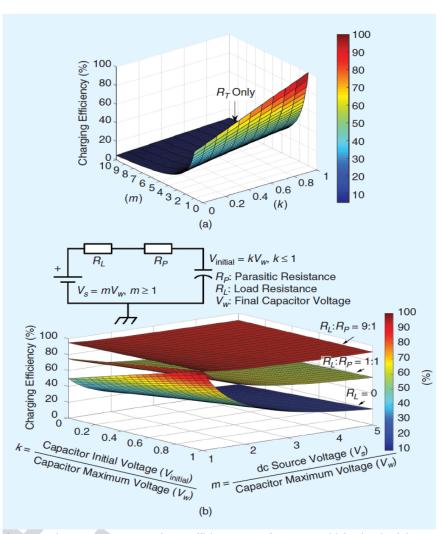



Figure 4 – The SCALOM concept. The (a) efficiency versus factors m and k for the circuit in Figure 3, and (b) overall efficiency improvement versus m and k with the insertion of useful resistor R_L into the loop [14].

SC assisted LED lighting for DC microgrid and renewable energy systems

SCALED Technique

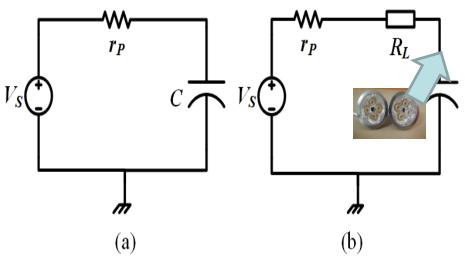


- LED lighting is internally operating with a DC supply
- DC products are more attractive for DCMG systems
- SC banks could replace battery banks, for environmentally friendly systems
- MPPT systems for battery banks will not work with SC banks (Impedance matching not possible)
- SCALED systems were developed to rescue this theoretical issue
- In SCALoM concept, we use a DC operable LED lamp load as the PEBB

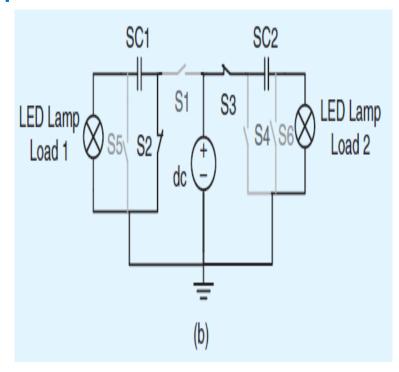

Implementation of SCALED system using two 12 V DC LED banks from a photovoltaic source

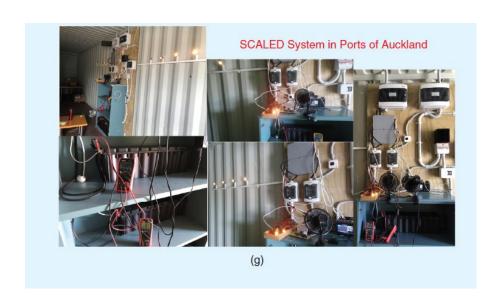SCALED System was tested in NZ at Auckland Port




- SCALED concept can be extended to DC whitegoods and air conditioners etc.
- This research is in progress now
- Details of the SCALED is published in IEEE/ IET

Ref: (2020) D. Jayananda, N. Kularatna & Steyn-Ross, D. A. Supercapacitor Assisted LED (SCALED) technique for renewable energy systems: A low-frequency design approach with short-term DC-UPS capability eliminating battery *IET Renewable Power Generation, Vol 14,* doi: 10.1049/iet-rpg.2019.1307 (2020), Early Access.

SC assisted high density inverter(SCHADI) technique

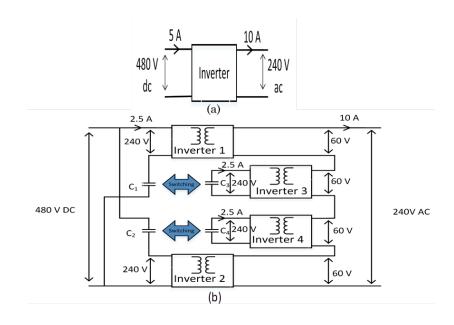- A loaded inverter is used in the charging path of a SC bank in an inverter system.
- The overall inverter is divided into several micro-inverters
- Outputs are series connected to get the required AC voltage
- SC banks keep powering half the micro-inverters
- Other half are directly powered through the charging loop



In SCAHDI also we use a SC and a useful resistor to circumvent losses

Conclusion

- When a capacitor becomes almost a million times larger it can be creatively used for very new circuit topologies and techniques
- These new techniques can help in
 - Reducing lost energy in power converters
 - Developing new surge protectors with low component count and better performance
 - Low voltage rapid energy transfer into flowing liquids
 - High density inverters
 - DC Microgrid applications for energy efficiency

What was presented is only the tip of the ice burg... Creative circuit designers can make us of commercial EDLCs in many more applications and much more versatile than in simple energy storage systems....

Thank you...

5th May 2020



